Evaluation

SECTION – A

Choose the correct answer

1. Which is a basic electronic circuit which operates on one or more signals?
   (A) Boolean algebra (B) Gate
   (C) Fundamental gates (D) Derived gates
2. Which gate is called as the logical inverter?
   (A) AND (B) OR
   (C) NOT (D) XNOR
3. A + A = ?
   (A) A (B) O
   (C) 1 (D) A
4. NOR is a combination of ?
   (A) NOT(OR) (B)NOT(AND)
   (C) NOT(NOT) (D) NOT(NOR)
5. NAND is called as …… Gate
   (A) Fundamental Gate (B) Derived Gate
   (C) Logical Gate (D) Universal gate

BUKQK5

SECTION-B

Very Short Answers

1. What is Boolean Algebra?
2. Write a short note on NAND Gate.
3. Draw the truth table for XOR gate.
4. Write the associative laws?
5. What are derived gates?

SECTION-C

Short Answers

1. Write the truth table of fundamental gates.
2. Write a short note on XNOR gate.
3. Reason out why the NAND an NOR are called universal gates?
4. Give the truth table of XOR gate.
5. Write the De Morgan's law.

SECTION - D

Explain in detail

1. Explain the fundamental gates with expression and truth table.
2. How AND and OR can be realized using NAND and NOR gate.
3. Explain the Derived gates with expression and truth table.

Chapter 2 Page 014-040.indd 40 3/24/2020 12:03:08 PM