
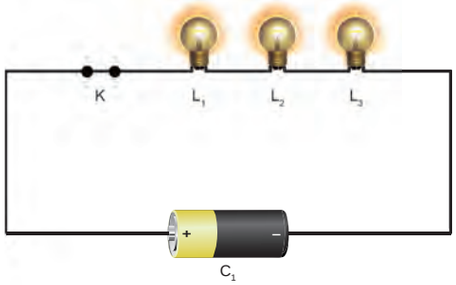
is damaged or disconnected, the entire circuit will not work.



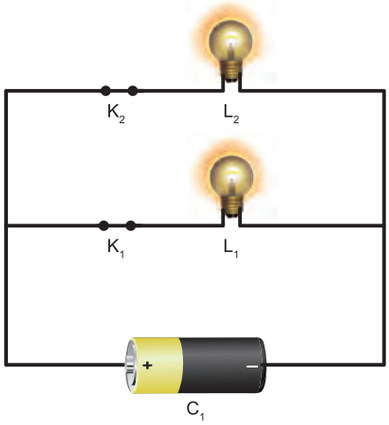3. Parallel Circuit



If two or more bulbs are connected in parallel in a circuit, then that type of circuit is called parallel circuit.

If any one of the bulb is damaged or disconnected the other part of the circuit will work. So parallel circuits are used in homes.



Symbols of Electric Components

In the circuits discussed above, we used the figures of electric components. Using electric components in complicated circuits is difficult. So, symbols of the components are used instead of figures. If these symbols used in electric circuits, even complicated circuits can be easily understood.

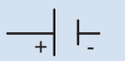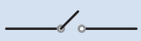Sl.no.	Electric component	Figure	Symbol	Remarks
1	Electric cell	 Cell		Longer terminal refers positive and shorter terminal refers negative.
2	Battery	 Battery		Two or more cells connected in series
3	Switch-open		 Open	Switch is in off position
4	Switch-closed		Closed	Switch is in on position
5	Electric bulb			The bulb does not glow
				The bulb glows
6	Connecting wires			Used to connect devices.

6th Science_IInd Term English Book_Unit_2.indd 22 25-03-2019 12.12.37 PM