
ICT Corner

Electricity

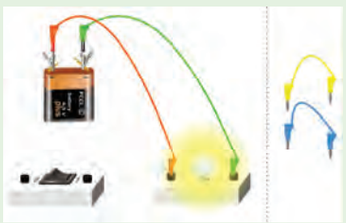Through this activity you will be able to form a simple circuit.



Step 1: Use the given URL in the browser. 'Simple Circuit will open.

Step 2: In right side of the activity window there are diagrams of some wires and in the left side diagrams of a battery, switch and a bulb are given.

Step 3: By using the mouse drag and drop the wires to the battery and switch to make connections. Click on the switch, if the circuit is formed correctly the bulb will glow.


Step 4: Use the second URL to try Series and parallel circuits.

Step 1





Step 2

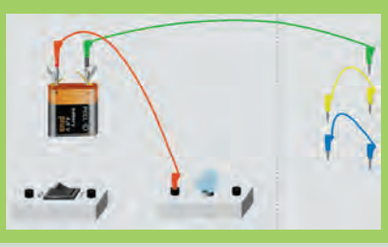

Step 3

Simple Circuit's URL:

http://www.physics-chemistry-interactive-flash-animation.com/electricity_electromagnetism_interactive/simple_circuit.htm

Series and parallel circuits url

http://www.physics-chemistry-interactive-flash-animation.com/electricity_electromagnetism_interactive/components_circuits_association-series_parallel.htm

B443_SCI_6_T2_EM

*Pictures are indicative only

6th Science_IInd Term English Book_Unit_2.indd 28 25-03-2019 12.12.46 PM