
V. Arrange in sequence

A CELL	A DEVICE	ELECTRICAL ENERGY
IS CALLED	IN TO	CHEMICAL ENERGY
THAT CONVERTS		

VI. Give very short answer

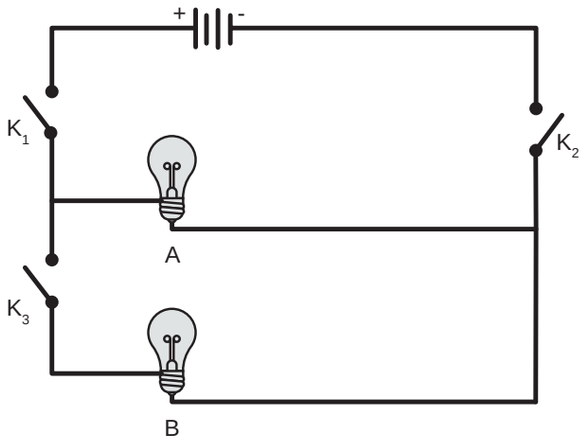1. In the given circuit diagram, which of the given switch(s) should be closed. So that only the bulb A glows.



2. Assertion (A) : It is very easy for our body to receive electric shock.

   Reason (R) : Human body is a good conductor of electricity.

   a. Both A and R are correct and R is the correct explanation for A.

   b. A is correct, but R is not the correct explanation for A.

   c. A is wrong but R is correct.

   d. Both A and R are correct and R is not the correct explanation for A.

3. Can you produce electricity from lemon?

4. Identify the conductor from the following figures.






5. What type of circuit is there in a torch light?

6. Circle the odd one out. Give reason for your choice.

   Switch, Bulb, Battery, Generator.

VII. Give short answer

1. Draw the circuit diagram for series connection.

2. Can the cell used in the clock gives us an electric shock? Justify your answer.

3. Silver is a good conductor but it is not preferred for making electric wires. Why?

VIII. Answer in detail

1. What is the source of electricity? Explain the various power stations in India?

2. Tabulate the different components of an electric circuit and their respective symbols.

3. Write short notes on conductors and insulators.

IX. Question based on Higher Order Thinking Skills

1. Rahul wants to make an electric circuit. He has a bulb, two wires, a safety pin and a piece of copper. He does not have any electric cell or battery. Suddenly he gets some idea. He uses a lemon instead of a battery and makes a circuit. Will the bulb glow?

6th Science_IInd Term English Book_Unit_2.indd 30 25-03-2019 12.12.47 PM