QUESTIONS

T3HPRZ

PART A

I. Choose the Best Answer

1. The output of a rectifier is

   a) Pulsating DC b) Pure DC c) Pure AC d) None of the above

2. Which of the following rectifier needs four diodes

   a) Half-wave rectifier b) Full-wave rectifier c) Bridge rectifier d) None of the above

3. The maximum efficiency of a half-wave rectifier is

   a) 20.3% b) 80.6% c) 50% d) 40.6%

4. Center tapped transformer is used in a rectifier.

   a) Bridge type b) Half-wave c) Full-wave d) None of the above

5. In a full wave rectifier, if AC supply is 50 Hz then AC ripple in the output is

   a) 50 Hz b) 100 Hz c) 25 Hz d) 200 Hz

6. A bridge type rectifier uses …….. diodes.

   a) Four b) Two c) Three d) One

7. For high voltage applications, we use

   a) Center tap rectifier b) Bridge rectifier

   c) Half-wave rectifier d) None of the above

8. In filter circuits, we generally use ……. capacitors.

   a) Mica b) Paper c) Air d) Electrolytic

9. In a half-wave rectifier, if AC supply is 50 Hz, then AC supply is 50 Hz, then AC ripple in the output is

   a) 100 Hz b) 25 Hz c) 50 Hz d) 12.5 Hz

10. The maximum rectification efficiency in full wave rectifier is

    a) 100% b) 81.2% c) 66.6% d) 40.6%

PART B

II. Answer in few sentences

1. What are the types of power conversion?
2. What is meant by PSU?
3. What is rectification?
4. Give the use of voltage regulator.
5. What is half-wave rectifier?
6. Give the uses of filter circuits.
7. Write short notes on an AC adapter.
8. Write important points of zener diode

ELEC_EQUIP_Chapter04.indd 96 11/10/2020 11:38:47 AM