PART C

III. Answer the following Questions.

1. Draw the block diagram of power supply unit and explain each block.
2. Explain half-wave rectifier with circuit diagram.
3. Explain the different types of power conversion.
4. Draw and explain CLC or pie filter.

PART D

IV. Answer the following Questions.

1. Draw the circuit diagram of full wave rectifier and explain its working function.
2. Draw the circuit diagram of bridge rectifier and explain its working function.
3. Explain the function of voltage doubler.

Answer Key

1. **(a)**	2. **(c)**	3. **(d)**	4. **(c)**	5. **(b)**
6. **(a)**	7. **(b)**	8. **(d)**	9. **(c)**	10. **(b)**

ELEC_EQUIP_Chapter04.indd 97 11/10/2020 11:38:47 AM