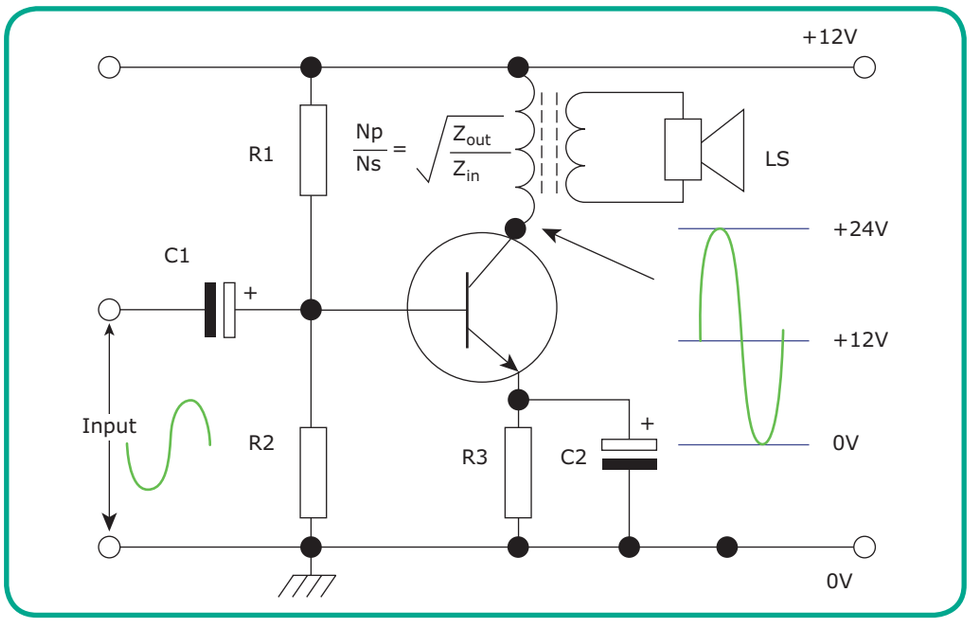


Figure 5.26 **Class A Power Amplifier**

two transistors are used in Class B operation as shown in Figure 5.27. One transistor amplifies the positive half cycle of the signal while the other amplifies the negative half cycle. The efficiency of Class B power amplifier is around 75%.

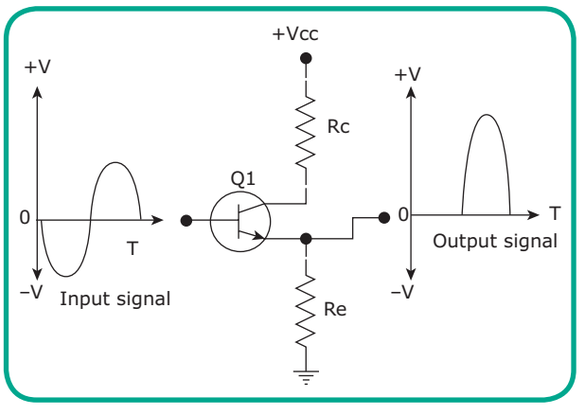


Figure 5.27 **Class B Power Amplifier**

5.12.3. Class C Power Amplifier

If the collector current flows for less than half cycle of the input signal, it is called as class C power amplifier. Class C power amplifiers are used as tuned amplifiers.

Class C amplifier has a conducting angle of class than 90° and is biased beyond cut- off. Figure 5.28 shows a Class C power amplifier with the associated input-output waveforms. The efficiency of Class C power amplifier is around 90%.

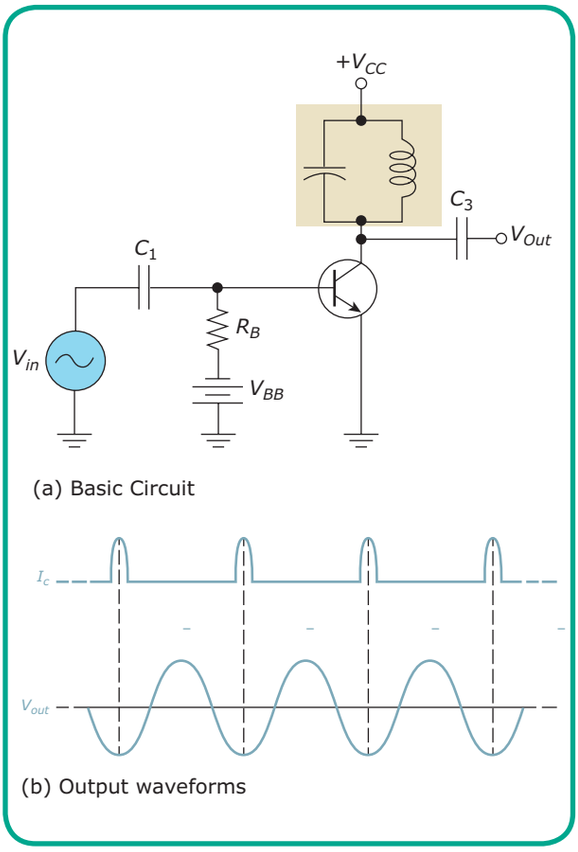


Figure: 5.28 **Class C Power Amplifier**

ELEC_EQUIP_Chapter05.indd 114 11/10/2020 11:41:49 AM