13. A complementary symmetry amplifier has

a) 1 PNP & 1 NPN transistor
b) 2 PNP transistor
c) 2 NPN transistor
d) 2 P channel FETS

14. The most commonly used transistor arrangement is ……..

a) Common emitter
b) Common base
c) Common collector
d) None of the above

15. Transistor operates in ……. biasing.

a) AC b) DC c) both AC and DC d) none of the above.

PART B

II. Answer in few sentences — 3 Marks

1. What is meant by a transistor?
2. Give the symbol of PNP and NPN transistor.
3. Write short notes on SMD transistor.
4. What are the various methods of transistor biasing?
5. Write about the different modes of transistor.
6. Define an amplifier
7. What is meant by voltage amplifier?
8. What is meant by power amplifier?
9. What is meant by feedback?
10. What are the types of feedback?
11. What is distortion?
12. Write down the types of distortion occurs in amplifier.

PART C

III Explain the following questions — 5 Marks

1. How will you identify the leads of transistor?
2. Explain the working principles of NPN transistor
3. Compare voltage amplifiers and power amplifiers.
4. What are the applications of transistor?

PART D

IV Explain briefly the following questions. — 10 Marks

1. Explain how transistor works as an amplifier.
2. Write some factors about transistor
3. Briefly explain about operating modes of transistor.
4. Explain the working principle of RC coupled amplifier.

ELEC_EQUIP_Chapter05.indd 120 11/10/2020 11:41:49 AM