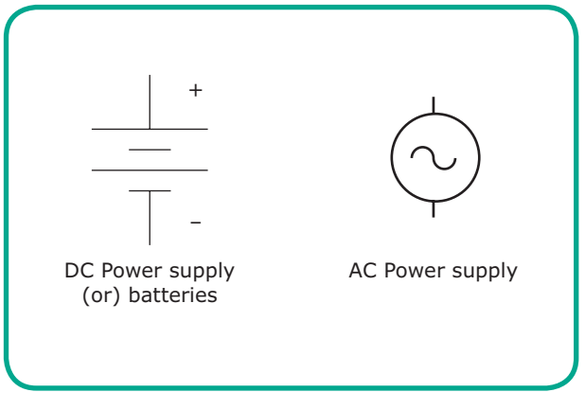


Figure 1.11 Electrical symbols

1.4.7 Circuit Diagram

An electrical technician can easily draw electrical connections if simplified symbols are used. Figure 1.12 shows a sample electrical circuit diagram.

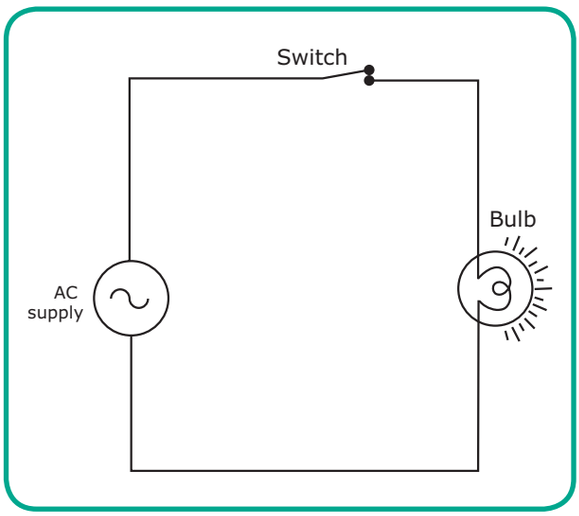


Figure 1.12 Example of a circuit diagram

A method of drawing electrical connections with simplified symbols is called circuit diagram.

1.4.8 Closed Circuit

A circuit connected in such a way to allow current flow through one or more loads with respect to the electrical supply. In a closed circuit, current will flow in the circuit as shown in Figure 1.13.

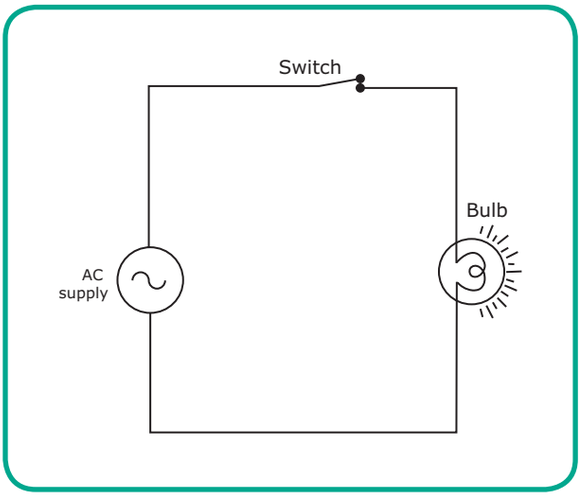


Figure 1.13 Closed circuit

1.4.9 Open Circuit

In a circuit, if there is no current flow due to disconnection of wire or switched-off condition, then the circuit is said to be open circuit. In an open circuit, no current flow in the circuit. Figure 1.14 shows a sample open circuit.

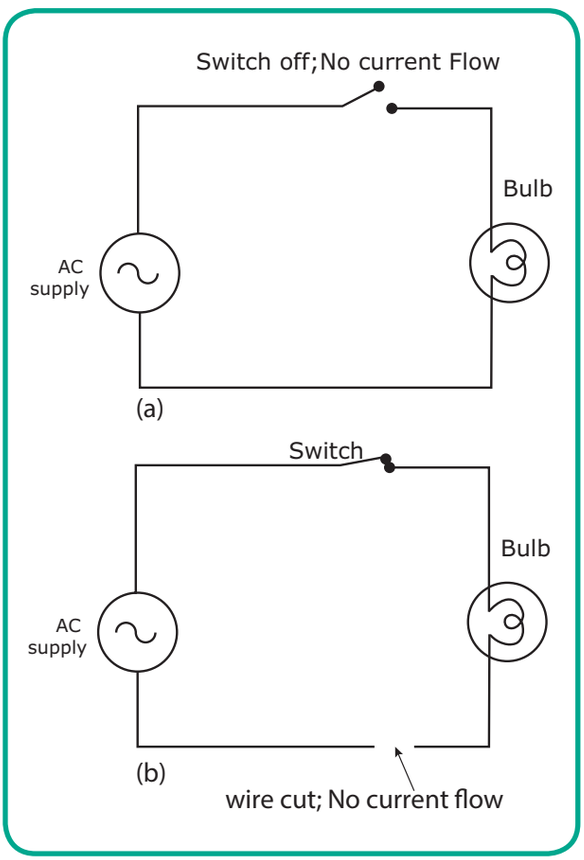


Figure 1.14 Open circuit

ELEC_EQUIP_Chapter01.indd 10 11/10/2020 12:22:39 PM