QUESTIONS

PART A

I Choose the correct answer 1Mark

1. An oscillator converts ……..
   a) AC power into DC power
   b) DC power into AC power
   c) Mechanical power into AC power
   d) None of the above

2. In an LC transistor oscillator, the active device is …….
   a) LC tank circuit
   b) Biasing circuit
   c) Transistor
   d) RC circuit

3. An oscillator produces ……. oscillations
   a) Damped b) Undamped c) Modulated d) None of the above

4. Hartley oscillator is commonly used in ……..
   a) Radio receivers
   b) Radio transmitters
   c) TV receivers
   d) TV transmitters

5. In a phase shift oscillator, we use …….. RC sections.
   a) Two b) Three c) Four d) One

6. In a phase shift oscillator, the frequency determining elements are ……..
   a) L and C b) R,L and C c) R and C d) R and L

7. In a crystal, the piezoelectric effect causes ……..
   a) A voltage is developed because of mechanical stress
   b) A change in resistance occurs because of temperature
   c) change in frequency occurs because of temperature
   d) None of the above

T4ZUNE

8. The crystal oscillator frequency is very stable due to …….. of the crystal.
   a) Rigidity b) Vibrations c) Low Q d) High Q

9. Astable multivibrator is …….. in any state.
   a) Stable b) Unstable c) Saturated d) Both (a) and (c)

10. Bistable multivibrator is …… in any state.
    a) Stable b) Unstable c) Saturated d) Independent

11. A monostable multivibrator has ……..
    a) No stable state
    b) One stable state
    c) Two stable state
    d) None of the above

12. Circuit which consists of a quasi-stable state is called …….
    a) Bistable circuit b) Monostable circuit c) Tristable circuit d) Tristate circuit

ELEC_EQUIP_Chapter07.indd 160 11/10/2020 11:46:13 AM