PART B

II Answer in few sentences — 3 Marks

1. What is an oscillator? How is it classified?
2. What is meant by piezoelectric effect?
3. How will you produce square wave?
4. What are the types of transistor oscillator?
5. What is positive feedback in an oscillator?
6. What is multivibrator? Give its types.
7. Give merits and demerits of crystal oscillator.

PART C

III Explain the following questions — 5 Marks

1. Explain damped and undamped oscillation with waveform diagram.
2. Draw and explain the essentials parts of an oscillator.
3. Write short notes on Astable and Monostable multivibrators.
4. Why positive feedback is much needed in an oscillator function? Justify it.

PART D

IV Answer the following questions in detail — 10 marks

1. Describe the construction and working principle of Hartley oscillator circuit.
2. Explain the working principle of RC phase shift oscillator with circuit diagram.
3. Draw and explain the working functions of crystal oscillator.
4. Explain the construction and working principle of bistable multivibrator with circuit diagram.

ANSWERS

1. (b)	2. (c)	3. (b)	4.(a)
5. (b)	6. (c)	7. (a)	8. (d)
9. (b)	10. (a)	11. (b)	12. (b)

ELEC_EQUIP_Chapter07.indd 161 11/10/2020 11:46:13 AM