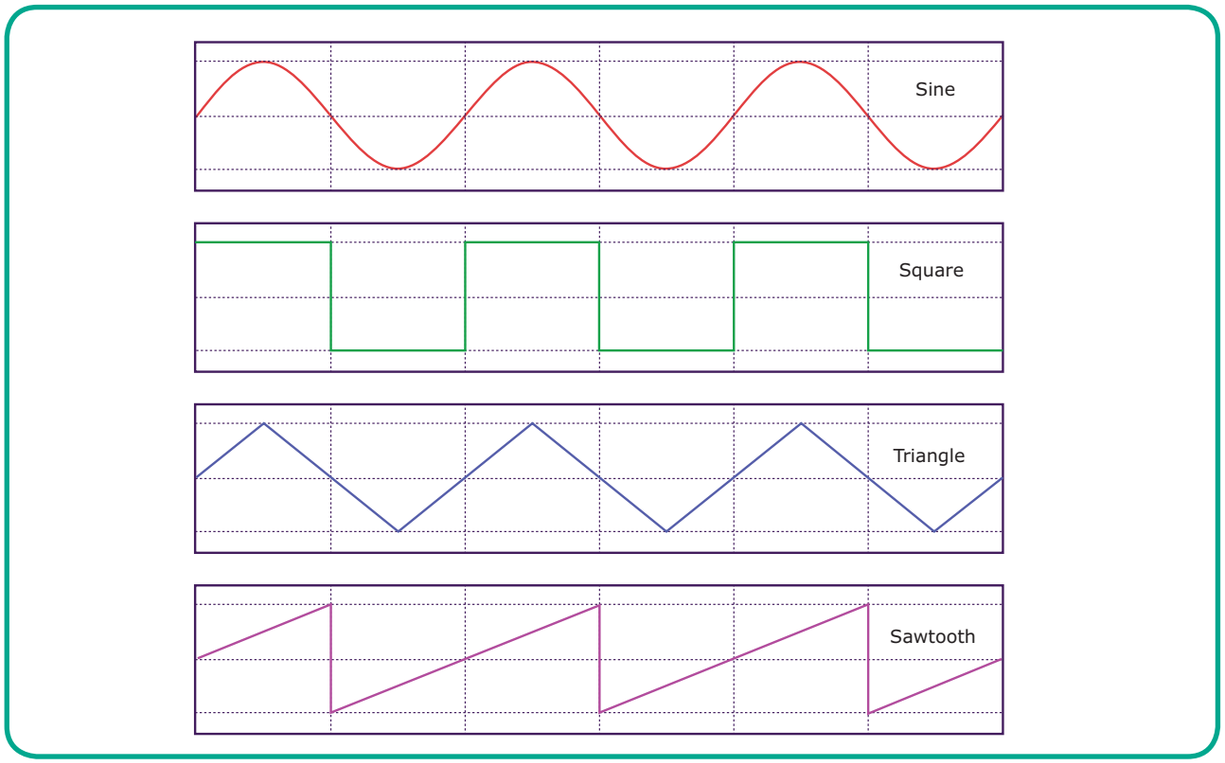


Figure 10.24(b) **Waveforms produced by Function Generator**

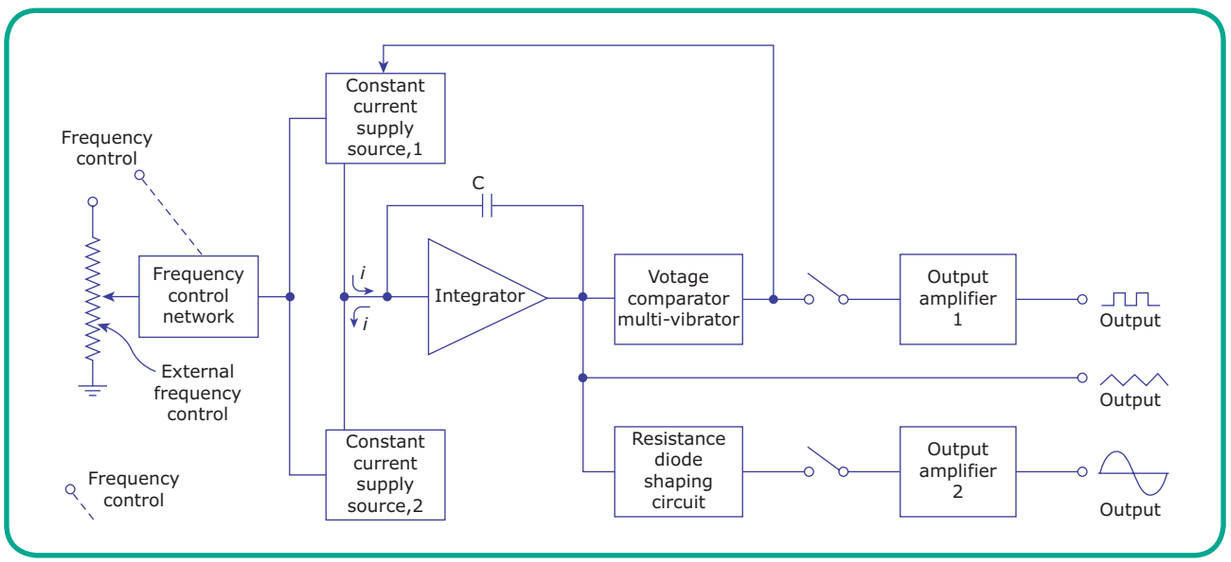


Figure 10.25 **Block Diagram of Function Generator**

1. Voltage comparator and multivibrator circuit.
2. Constant current source circuits.
3. Resistance and diode shaping circuit.
4. Frequency control network
5. Output amplifiers

Using these circuits, a function generator produces various signals and are listed below.

1. Sine Waves
2. Triangular Waves
3. Square Waves
4. Saw Tooth Waves

ELEC_EQUIP_Chapter10.indd 218 11/10/2020 11:55:38 AM