S.No	V_{in} (Volts)	V_1	V_2	V_3	I
1.	2				
2.	4				
3.	6				
4.	8				
5.	10				

Resistors in parallel

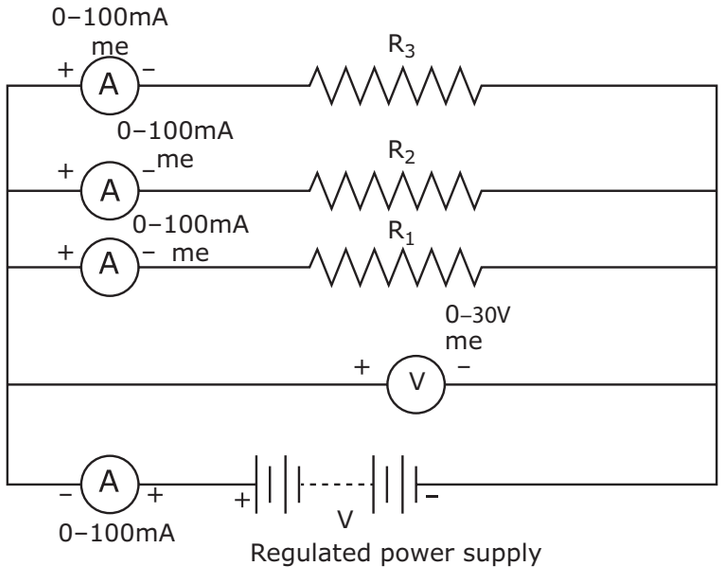


Fig 5.2 **Resistors in Parallel**

1. Connect the components as per the circuit diagram.
2. Switch ON the power supply and give fixed DC voltage to the circuit.
3. Measure the current flow through each resistor (I_1, I_2,I_3).
4. Measure the supply voltage (V).
5. Repeat the same procedure for different input DC voltages.
6. Tabulate the readings

S.No	V_{in} (Volts)	I_1	I_2	I_3	I
1.	2				
2.	4				
3.	6				
4.	8				
5.	10				

Result:

The different voltage and current values are measured when resistors are connected in series and parallel.

Activity :

Relationship between the voltage, current and resistance using a graph diagram.

EE_Practicals_English Version.indd 247 11/10/2020 12:17:47 PM