1. Select the multimeter in X 1 ohm's range.
2. Connect both probes with both ends of the primary coil. Observe the value of meter reading.
3. If the needle of the meter shows few hundred ohms, the primary coil is said to be in good condition.
4. If the needle of the meter shows ∞ Ω, the primary coil is said to be open.
5. Connect both probes with both ends of the secondary coil. Observe the value of meter reading.
6. If the needle of the meter shows few ohms, the secondary coil is said to be in good condition.
7. If the needle of the meter shows ∞ Ω, the secondary coil is said to be open.

Testing of Relay Contacts

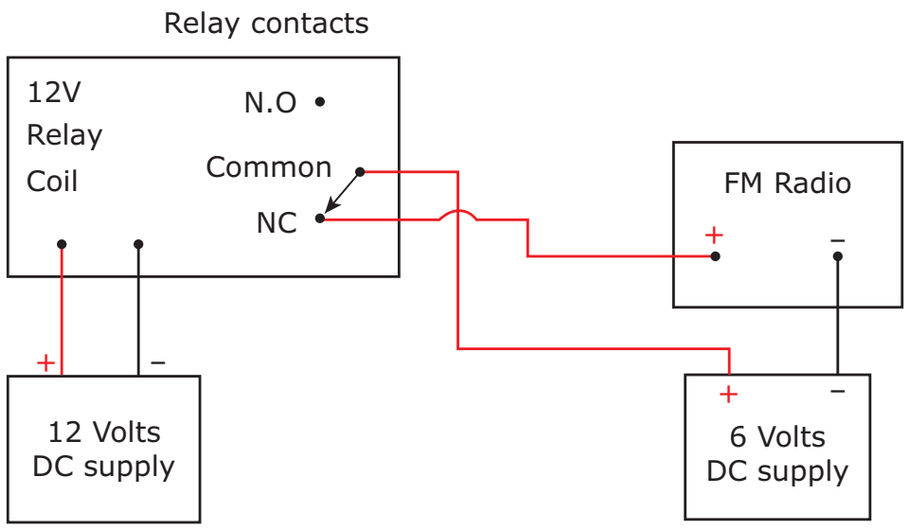


Fig 6.4 **Testing of Relay**

1. Connect the relay coil with 12 volts dc supply.
2. Connect the relay N.C. switch with +ve input of FM radio (Load).
3. While giving the 12V supply, the Relay coil gets magnetized. Coil attracts the small metal lever, which brings the relay contacts to ON position.
4. You can hear the click sound from relay. It denotes the N.C terminal gets on.
5. The FM radio will work, after the relay turns on the relay switch.

EE_Practicals_English Version.indd 250 11/10/2020 12:17:47 PM