7 TESTING OF DIODES AND TRANSISTORS

Aim

Testing of diodes and transistors using Analog Multimeter

Apparatus required

S.No	Name of the apparatus / Component	Range/Value	Quantity
1.	Multimeter (Analog)	--	1 No
2.	Diode	IN 4007	1 No
3.	Zener Diode	6V or 12 V	1 No
4.	Transistor	BC 548 (NPN)	1
5.	Transistor	BC 558 (PNP)	1

Circuit Diagram

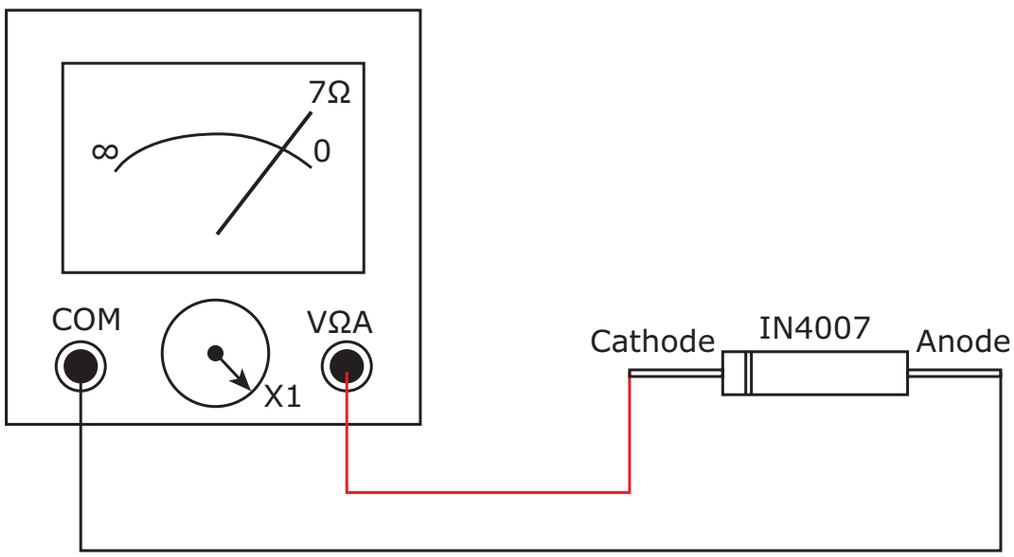


Fig 7.1 Diode testing

EE_Practicals_English Version.indd 252 11/10/2020 12:17:47 PM