8 CONSTRUCTION OF 6V DC POWER SUPPLY (BRIDGE RECTIFIER)

Aim:

To construct the 6V DC power supply (bridge rectifier) and measure the input AC main voltage and output DC voltage.

Apparatus / Components Required:

S. No	Name of the apparatus / Components	Range / Value	Quality
1.	Multimeter	-	1 No.
2.	Step down transformer	0 – 6V, 1A	1 No.
3.	Mains cord	-	1 No.
4.	Diode	IN 4007	4 Nos.
5.	Resistor	100Ω, 1W	1 No.
6.	Electrolytic capacitor	1000μ*F* / 25V	2 Nos

CIRCUIT DIAGRAM

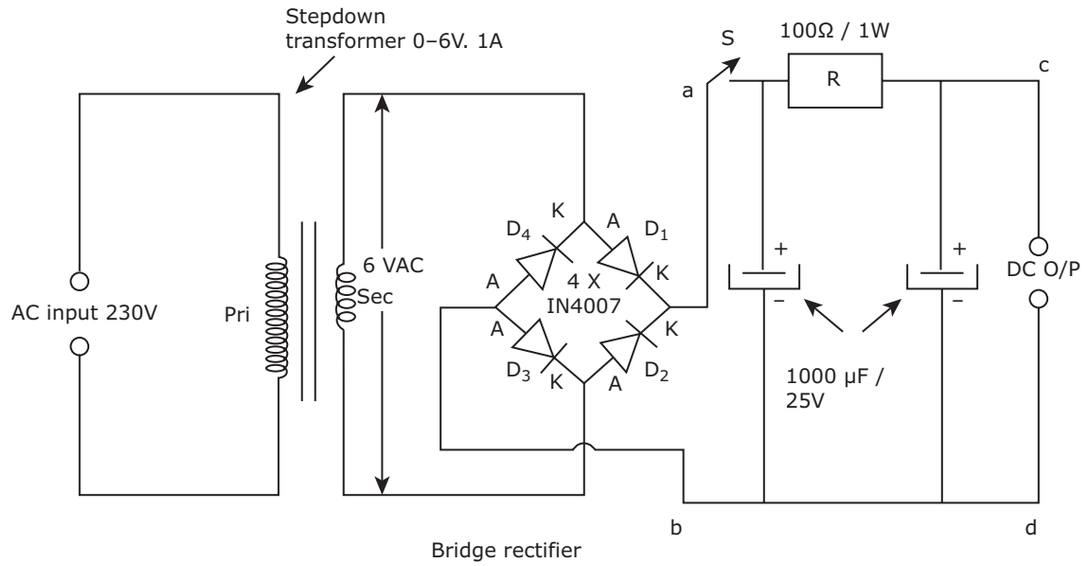


Fig 8.1 Power supply Circuit

EE_Practicals_English Version.indd 256 11/10/2020 12:17:48 PM