Procedure:

1. Construct the circuit as per the circuit diagram.
2. Switch ON the power supply.
3. Measure the input AC secondary voltage and output DC voltage using multimeter.
4. Then switch off the power supply and disconnect the circuit.

S.No	Voltage	Meter Reading
1	AC Input voltage (Secondary)	
2	DC Output voltage (with out filter)	
3	DC Output voltage (with filter)	

Activity :

Assemble an eleminator using 1.5V to 12V tapped transformer and 4 diodes, measure the voltage

Voltage terminal	Output Voltage	
	Without load	With load

Result:

The Construction of Bridge rectifier is done and input/output voltages are measured.

EE_Practicals_English Version.indd 257 11/10/2020 12:17:48 PM