9 VOLTAGE REGULATOR USING IC 7812

Aim:

To construct the IC based voltage regulator.

Apparatus / Component's required:

S.No	Name of apparatus / components	Range / value	Quantity
1.	Regulated power supply	0-30 V DC	1 No.
2.	Multimeter	-	2 No.
3.	IC 7812	-	1 No.
4.	Electrolytic capacitor	100 µF / 25V	1 No.
5.	Disc capacitor	0.1 µF	1 No.

CIRCUIT DIAGRAM

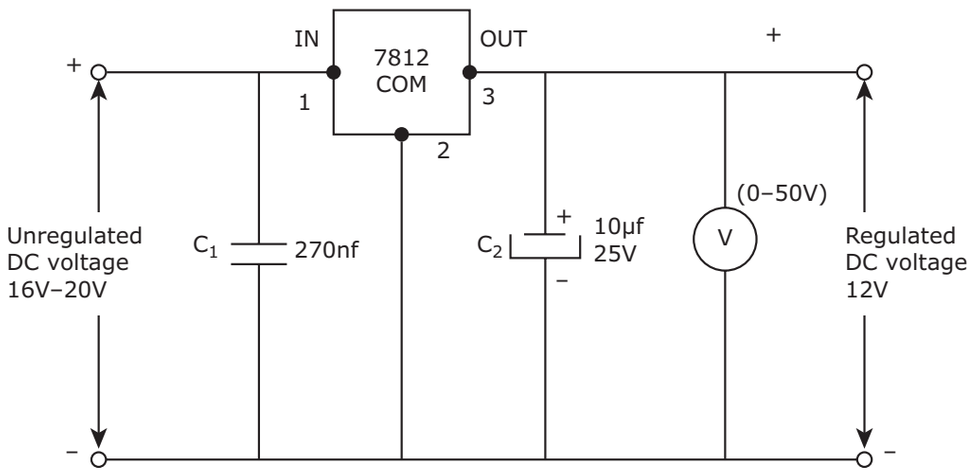


Fig 9.1 IC-Voltage Regulator

Procedure:

1. Connect the components as per the circuit diagram
2. Apply 16 to 20 volts unregulated dc voltage to the first pin (input) of IC to get 5 different readings.
3. Measure and tabulate the unregulated input voltage and regulated output voltage.
4. Switch OFF the supply and disconnect the circuit.

EE_Practicals_English Version.indd 258 11/10/2020 12:17:48 PM