Tabular column

S.No	DC input voltage in volts	DC Output voltage in volts
1.		
2.		
3.		
4.		
5.		

Result:

Thus, the IC based voltage regulator is constructed and input, output voltages are tabulated.

EE_Practicals_English Version.indd 259 11/10/2020 12:17:48 PM