CONSTRUCTION OF COMMON EMITTER (CE) AMPLIFIER CIRCUIT

10

Aim :

To Construct the Common Emitter (CE - NPN) amplifier circuit

Apparatus Required

S.No	Apparatus/components Required	Range/ Value	Quantity
1	Transistor	BC 548	1
2	Resistor	47 KΩ, 10KΩ, 820Ω, 180Ω	Each one
3	Regulated Power supply	0 – 30 V DC, 1 A	1
4	Bread board	----	1
5	Electrolytic capacitor	100 µF/16 V	1
6	Electrolytic capacitor	1 µF/16 V	2
7	Multimeter	----	1

Procedure

1. Connect the components in bread board as per the circuit diagram.
2. Give supply to the circuit.
3. Measure and tabulate the voltages of B + , Emitter , Base , Collector.

EE_Practicals_English Version.indd 260 11/10/2020 12:17:48 PM