Circuit diagram

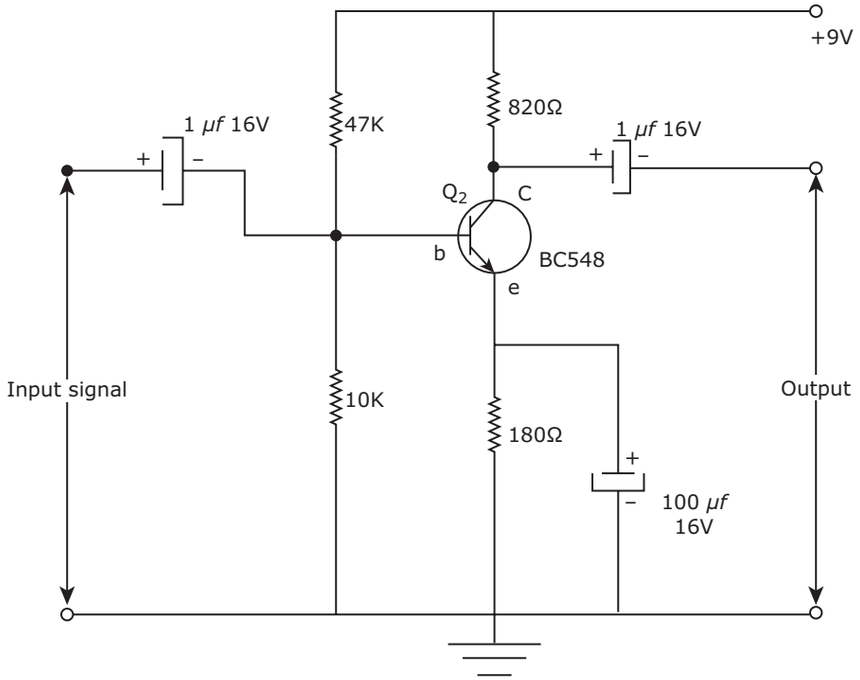


Fig 10.1 Common Emitter amplifier circuit – single stage

Tabular Column

Sl.No.	Terminals to be measured	Meter Reading
1	B +	
2	- ve to Emitter	
3	- ve to Base	
4	- ve to Collector	
5	Emitter to Base	
6	Emitter to collector	

Activity :

Connect a speaker and check its sound, find the waveform using oscilloscope.

Result:

The construction and measuring of Common Emitter (CE) amplifier circuit is studied.

EE_Practicals_English Version.indd 261 11/10/2020 12:17:48 PM