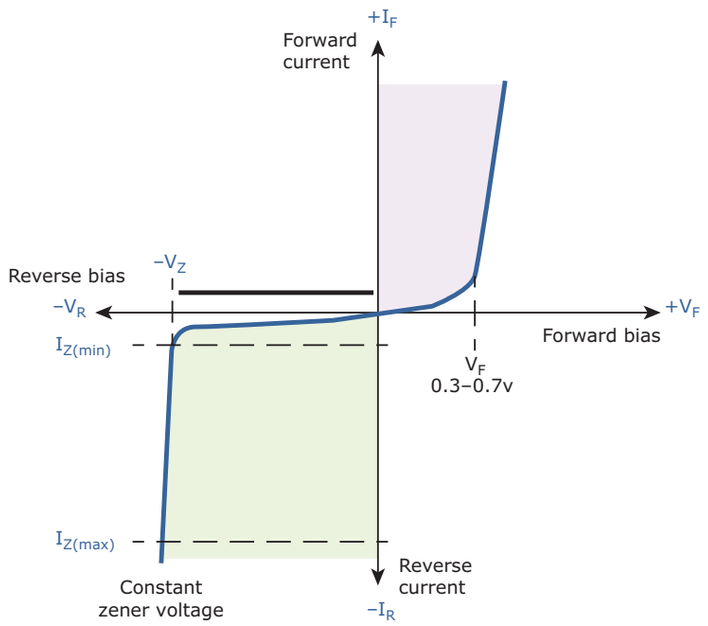


S.No	Voltage (V_R) in volts	Current (I_R) in mA
1	0.5	
2	1.0	
3	1.5	
4	2.0	
5	2.5	
6	3.0	
7	3.5	
8	4.0	
9	4.5	
10	5.0	
11	5.5	
12	6.0	
13	6.5	
14	7.0	

Activity :

Draw a graph using the tabulated voltages and ponit out the break down voltage.

Result

Thus the V-I characteristics of Zener diode is studied.

EE_Practicals_English Version.indd 263 11/10/2020 12:17:48 PM