
AND Gate

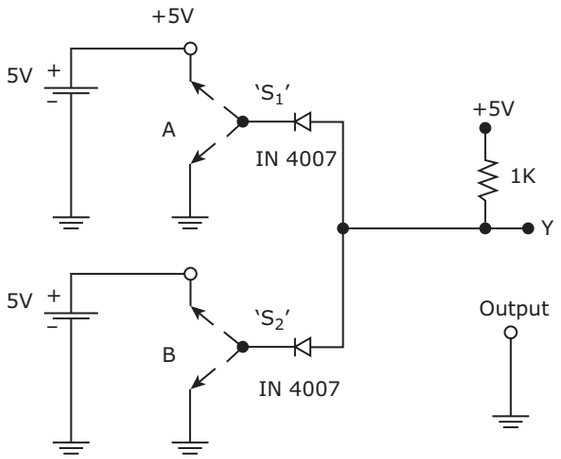


TRUTH TABLE

AND - Gate		
Input		Output
A	**B**	**Y=A·B**
0	0	0
0	1	0
1	0	0
1	1	1

Fig 12.2 **AND Gate**

NOT Gate

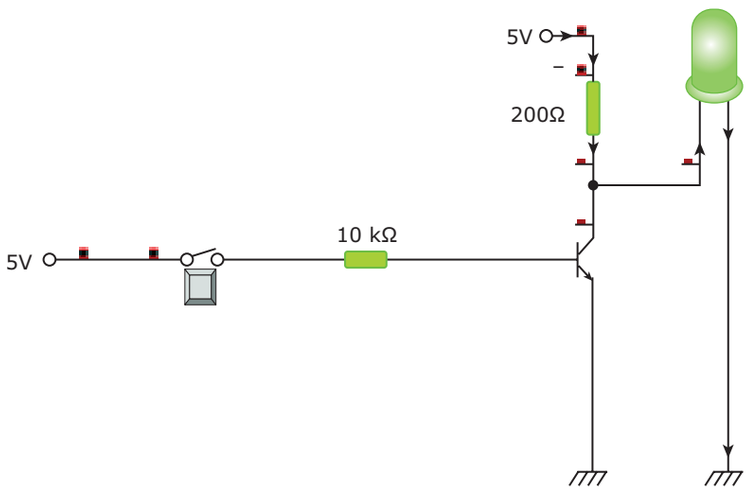

TRUTH TABLE

NOT - Gate	
Input **A**	**Output** **Y=Ā**
0	1
1	0

Fig 12.3 **NOT Gate**

Activity :
Construct the above gates. check and compare with truth table.

Result:

Thus AND, OR, NOT gates are constructed and their truth tables verified.

Any one of the following ideas may be selected as Project to be done. **(5 Marks)**

1. 1. Blinking LED decorative lamps using Astable multivibrator (transistorised circuit).
2. 2. Logic Probe Tester.
3. 3. To display Numbers from 0 to 9 in a Seven segment display.
4. 4. To display any 5 Tamil letters in an LED matrix display.
5. 5. To display any 5 English letters in an LED matrix display.

OR

1. Any other project, the concerned vocational teacher is willing to do.

EE_Practicals_English Version.indd 265 11/10/2020 12:17:49 PM