POWER SUPPLY

CHAPTER 4

திறனறிந்து சொல்லுக சொல்லை அறனும்
பொருளும் அதனினூஉங்கு இல். குறள் –644

T3MTQC

விளக்கம்:
சொல்லின் திறத்தை அறிந்து சொல்லை வழங்க வேண்டும், அத்தகைய சொல்வன்மையை விடச் சிறந்த அறமும் பொருளும் இல்லை.

English Couplet 644:

Speak words adapted well to various hearers' state;
No higher virtue lives, no gain more surely great.

Couplet Explanation:
Understand the qualities (of your hearers) and (then) make your speech; for superior to it, there is neither virtue nor wealth.

CONTENT

4.1 Introduction
4.2 Basics of power supply
4.3 Rectifier
4.4 Half wave rectifier
4.5 Full wave rectifier
4.6 Bridge rectifier
4.7 Filter circuits
4.8 Voltage regulator
4.9 Voltage doubler
4.10 Adapter

LEARNING OBJECTIVES

After the completion of this Chapter, the students can

1. **Identify the various sections of a power supply**
2. **State the purpose of each section of a power supply**
3. **Describe the purpose of various types of rectifier circuits used in power supply.**
4. **Describe the purpose of the various types of filter circuits used in power supply**
5. **Describe the function of voltage doubler.**
6. **Calculate the peak value of the output voltage of half-wave and full-wave rectifier given in the R.M.S input voltage.**

ELEC_EQUIP_Chapter04.indd 83 11/10/2020 11:38:44 AM