

# Electricity

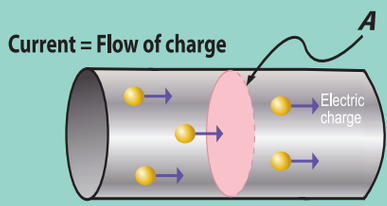**Electric current is the flow of electric charges, typically through wires, conductors and electric devices**



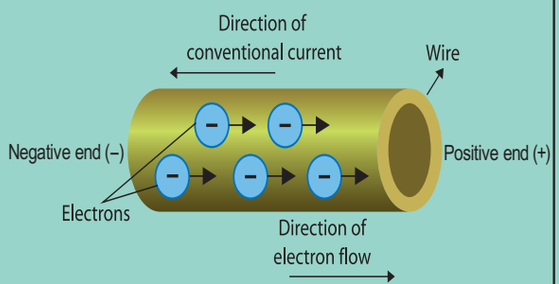
## Conventional current and Electric current




**Conventional current**

**Conventional current flow is from positive (`+` ) to negative (`-`)**


**Electric current**

**Electric current flow is from (`-`)negative to (`+` ) positive**

**Electric current I = Q/t**


## Water current vs electric current - Analogy

**Water current in a river**

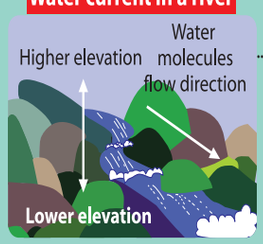



water molecules flow towards a point of lower elevation

**Electric current in a wire**

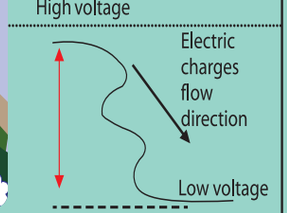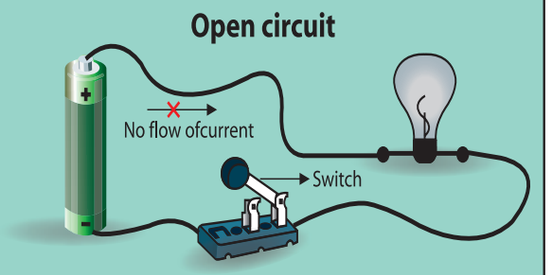

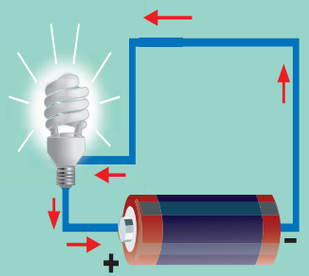

Electric charges flow towards a point of lower voltage

## Open circuit



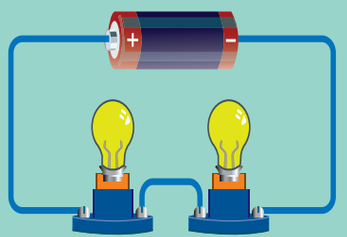

An incomplete electrical circuit in which no current flows

## Closed circuit




An electric circuit providing an uninterrupted endless path for the flow of current

## Series circuit



Circuit that has only one closed path through which the electric current flows

## Parallel circuit

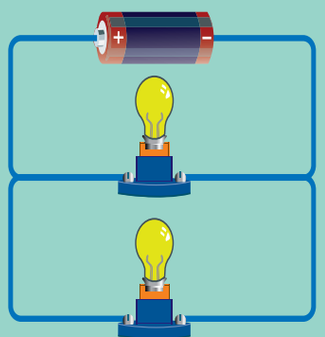

Circuit that Offers more than one path for the flow of electric current



VII Std Science Term-2 EM Unit 2 Folder.indd 24 20-07-2019 1.47.13 PM