VIII. Short Answer

1. Define an electric current.
2. Differentiate parallel and serial circuits.
3. Define electrical conductivity.

IX. Long Answer

1. Explain the construction and working of an Telephone.
2. Explain the heating effect of electric current.
3. Explain the construction and working of a dry cell.

X. Higher Order Question

A student made a circuit by using an electric cell, a switch, a torch bulb (fitted in the bulb holder) and copper connecting wires. When he turned on the switch, the torch bulb did not glow at all. The student checked the circuit and found that all the wire connections were tight.


- ❖ What could be the possible reason for the torch bulb not glowing even when the circuit appears to be complete?

XI Picture based Questions

1. Three conductors are joined as shown in the diagram

The current in conductor RS is 10 A. The current in conductor QR is 6 A. What will be the current in conductor PR

a) 4 A
b) 6 A
c) 10 A
d) 16 A

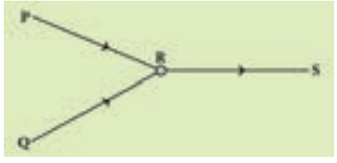


2. Draw the circuit diagram for the following series connection




3. Study the electric circuit below. Which of the following switches should be closed so that only two bulbs will light up

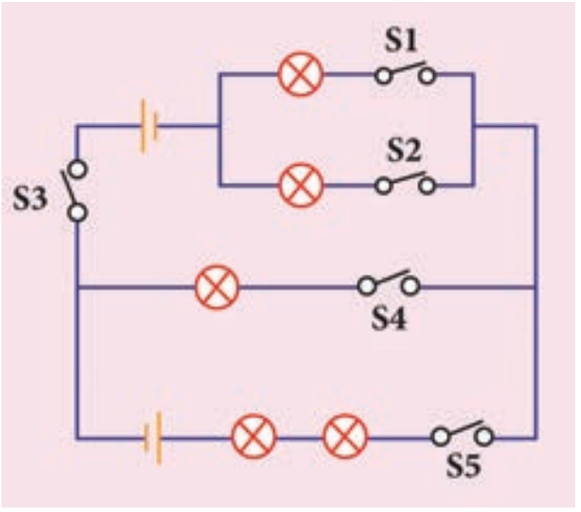a) S1,S2 and S4 only
b) S1, S3 and S5 only
c) S2, S3 and S4 ony
d) S2, S3 and S5 only



4. Study the three electric circuits below. Each of them has a glass rod (G), a steel rod (S), and a wooden rod (W).
In which of the electric circuits would the bulb not light up .

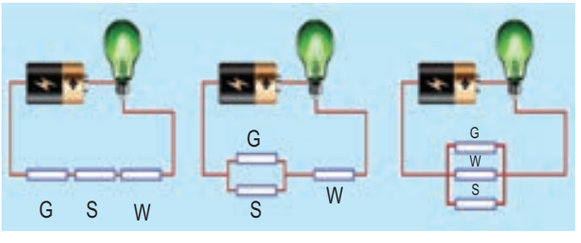a) A only
b) C only
c) A and B only
d) A , B and C



VII Std Science Term-2 EM Unit 2 Folder.indd 34 20-07-2019 1.47.18 PM