source of electrical energy is converted into other form of energy like light, heat, mechanical and so on. For each coulomb of charge passing through the light bulb (or any appliances) the amount of electrical energy converted to other forms of energy depends on the potential difference across the electrical device or any electrical component in the circuit. The potential difference is represented by the symbol V.

$$V = W/q$$

where, W is the work done, i.e., the amount of electrical energy converted into other forms of energy measured in joule and q is amount of charge measured in coulomb. The SI unit for both e.m.f and potential difference is the same i.e., volt (V).


Problem 5

A charge of 2×10^4 C flows through an electric heater. The amount of electrical energy converted into thermal energy is 5×10^6 J. Compute the potential difference across the ends of the heater.

Solution:

$V = W/q$ that is 5×10^6 J / 2×10^4 C = 250 V

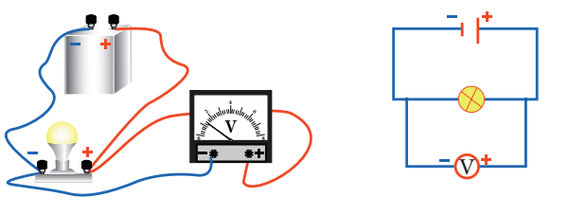Voltmeter is an instrument used to measure the potential difference. To measure the potential difference across a component in a circuit, the voltmeter must be connected in parallel to it. Say, you want to measure the potential difference across a light bulb, you need to connect the voltmeter as given in Figure 4.8.



(a) Actual setup (b) Circuit diagram

Figure 4.8 Connection of voltmeter in a circuit

Note the positive (+) red terminal of the voltmeter is connected to the positive side of circuit and the negative (–) black terminal is connected to the negative side of the circuit across a component (light bulb in the above illustration).

4.2.5 Resistance

The Resistance (R) is the measure of opposition offered by the component to the flow of electric current through it. Different electrical components offer different electrical resistance.

Metals like copper, aluminium etc., have very much negligible resistance. That is why they are called good conductors. On the other hand, materials like nicrome, tin oxide etc., offer high resistance to the electric current. We also have a category of materials called insulators; they do not conduct electric current at all (glass, polymer, rubber and paper). All these materials are needed in electrical circuits to have usefulness and safety in electrical circuits.

The SI unit of resistance is ohm with the symbol (Ω). **One ohm is the resistance of a component when the potential difference of one volt applied across the component drives a current of one ampere through it.**

We can also control the amount of flow of current in a circuit with the help of resistance. Such components used for providing resistance are called as 'resistors'. The resistors can be fixed or variable.

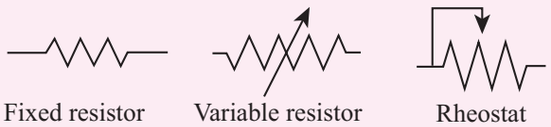


Figure 4.9 Circuit symbol for resistor

Fixed resistors have fixed value of resistance, while the variable resistors like rheostats can be used to obtain desired value of resistance (Fig. 4.9).

IX_SCI_EM_Unit-04_PHY.indd 43 12-02-2020 14:14:25