ELECTRIC CIRCUIT

The circuit is defined as the current flows from the supply points through the load to complete the path.

Types of circuits:

1. Series circuit
2. Parallel circuit

Series Circuit

When a circuit is made up of two or more resistance it is connected in series, it is known as series circuit.

$$V = V_1 + V_2 + V_3$$

$$R = R_1 + R_2 + R_3$$

I = same for all elements.


Parallel Circuit

When two or more resistances are connected parallelly to each other with same starting and ending points, this circuit is known as parallel circuit.

$$V = V_1 = V_2 = V_3$$

$$I = I_1 + I_2 + I_3$$

$$1/R = 1/R_1 + 1/R_2 + 1/R_3$$

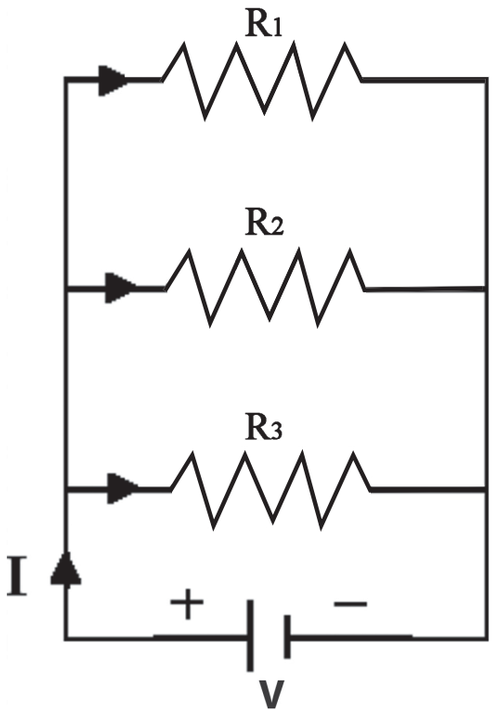


Parallel Circuit

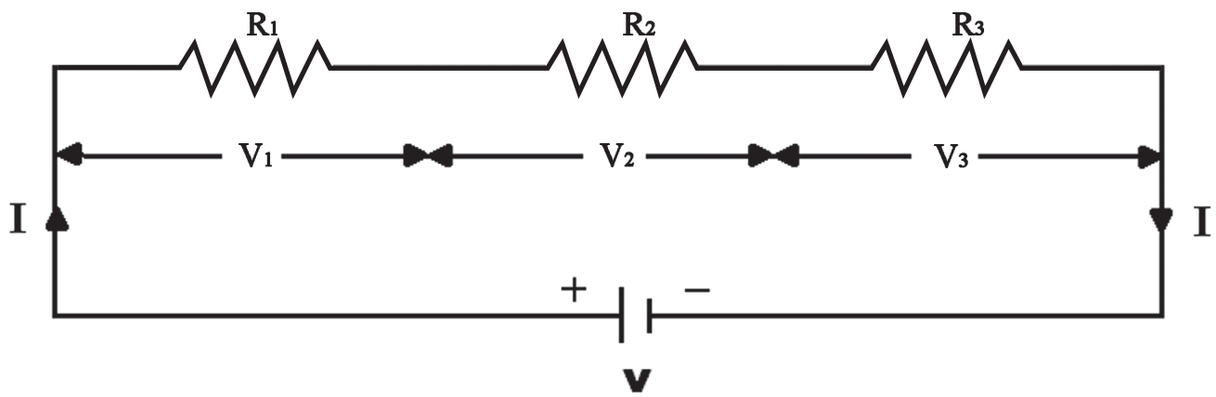10.3 MAGNETISM

Magnetism is a force field that acts on some materials. Physical device which possesses this force is called Magnet.

The force to attract iron is known as Magnetism. The substance which possesses magnetism is called Magnet. The materials attracted by magnet is known as Magnetic materials.



Series Circuit

GM_Chp10.indd 129 14-02-2019 11:46:20