PART: B

3 Marks

II. Answer the following questions in one or two sentences:

8. What is electric current?
9. What do you mean by Electric resistance?
10. State ohm's law
11. State Faraday's first law
12. State Faraday's second law
13. List out the types of electrical motors
14. What are the types of starters used in induction motors?
15. What are the safety devices fitted in starters to protect the induction motors?
16. What is the need of a starter in a electric motor?

PART: C

5 Marks

III Answer the following questions in about a page?

17. Series circuit, parallel circuit-explain with neat sketch
18. Explain Flemming's Right Hand Rule with illustration
19. Explain Flemming's Left Hand Rule with illustration
20. Compare D.C with A.C

PART: D

10 Marks

IV. Answer the following questions in detail:

21. Differentiate between squirrel cage induction motor and a slip ring induction motor?
22. Explain a D.O.L starter with neat sketch?
23. Explain a neat diagram of a star-delta starter.
24. Explain a A.C single phase capacitor start motor with a neat sketch.

GM_Chp10.indd 142 14-02-2019 11:46:24