
Points to Remember:

1. Transfer electrical energy from one circuit to another circuit.
2. It works without changing the frequency.
3. Transformer works on the principle of mutual induction.
4. Transformer works on AC supply only, not in DC.
5. E.M.F induced in primary winding $= (E_1) = 4.44\ N_1\ f\emptyset_m$ Volts.
6. E.M.F induced in secondary winding $= (E_2) = 4.44\ N_2\ f\emptyset_m$ Volts.
7. % Efficiency $(\eta) = \frac{\text{output power}}{\text{input power}} \times 100$
8. Voltage transformation ratio (K)

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = k = \frac{V_2}{V_1} = \frac{I_1}{I_2}$$

Activities

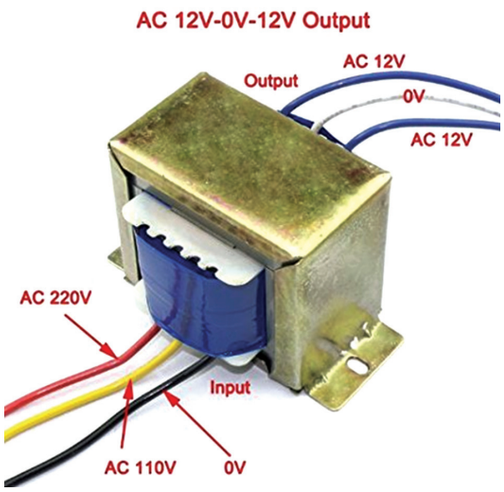1. Measure the output voltage of given transformer below.
2. Construct 6V transformer with centre tapping connection.
3. Calculate the losses occuring in the transformers by OC and SC tests.



GLOSSARY

Transformer	—	மின்மாற்றி
Step-up transformer	—	உயர்வழுத்த மின்மாற்றி
Step-down transformer	—	குறைவழுத்த மின்மாற்றி

EMA_English_Chp06.indd 101 11/9/2020 3:19:38 PM