Q A PART C

Mark 5

Answer the following questions not exceeding one page

1. Briefly Explain "Atomic Structure".
2. Explain the use of Filter circuits.

Q A PART D

Mark 10

Answer the following questions not exceeding two page

1. Explain half-wave rectifier with neat circuit diagram.
2. Explain full-wave bridge rectifier with neat circuit diagram.
3. Explain the operation of Zener diode.
4. Explain the working of pnp transistor.
5. Explain the working of npn transistor.
6. What are the advantages of using (i) LED (ii) LCD?
7. Explain seven segment display with diagram.

Reference Books

1. 'A text book of Electrical Technology' Volume I and Volume IV by B.L. Theraja and A.K. Theraja, S. Chand & Company Ltd.
2. Principles of Electronics by V.K. MEHTA and SHALU MEHTA, S. Chand & Company Ltd.

Internet Resource

www.electrical4u.com
www.electronics.com

EMA_English_Chp10.indd 168 12/17/2019 5:54:25 PM