
Aim

To determine the resistance value of two given coils of wire by using Ohm's Law.

Apparatus Required

S No	Name	Quantity
1	Battery -12V	1
2	Plug Key	1
3	Rheostat	1
4	Resistances	2
5	Voltmeter - 0-10V	1
6	Ammeter - 0-1A	1
7	Connecting Wires or Cord	As Required

Connection Diagram

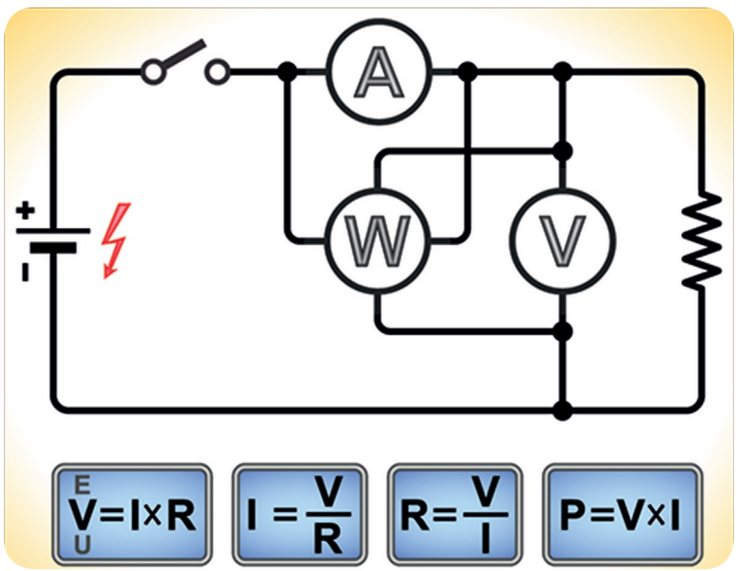

Ohm's Law

At constant temperature, the current flowing through the conductor is directly proportional to the voltage across it and inversely proportional to the resistance of the conductor.

$$I = \frac{V}{R}$$

$$V = I \times R$$

$$R = \frac{V}{I}$$

Where

V= Voltage in volts

I = Current in amps

R = Resistance in ohms

EMA_English_Practical.indd 206 11/9/2020 3:56:10 PM