
Procedure

- The first coil R_1 is connected as shown in the circuit diagram.
- After checking the connection, close the plug key.
- Adjust the rheostat.
- The corresponding voltmeter and ammeter readings are noted and are tabulated.
- By using the formula $R_1 = \frac{V}{I}$, the value of resistance is determined.
- Similarly, the second coil R_2 is connected as shown in the circuit diagram.
- After checking the connection, close the plug key.
- Adjust the rheostat.
- The corresponding voltmeter and ammeter readings are noted and are tabulated.
- By using the formula $R_2 = \frac{V}{I}$, the value of resistance is determined.

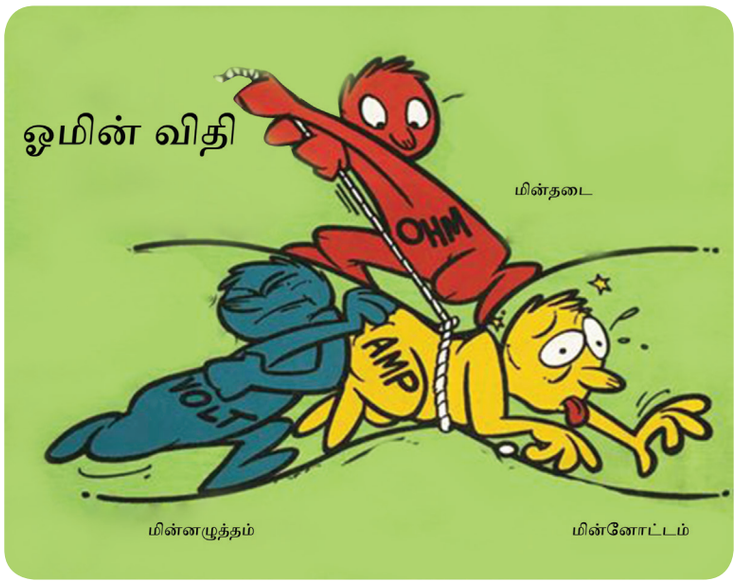

To Find R_1

S No	Ammeter reading 'I' in ampere	Voltmeter reading in 'V' volts	Resistance $R_1 = \frac{V}{I}$ Ohms
1.			
2.			
3.			
4.			
5.			

Mean R_1 = _____

EMA_English_Practical.indd 207 11/9/2020 3:56:10 PM