Connection Procedure

1. Provide holes in the wooden board at the required places wherever necessary.
2. Fix the switches, socket, fuse indicator, ammeter and voltmeter properly.
3. Give connection to all accessories as per the connection diagram.
4. Connect the power cord properly.

Testing Procedure

1. Connect the given appliances to the test lamp by series.
2. Lamp lighting and faults

S No	Lamp Lighting	Fault
1	Glows Dimly	No fault. Appliance "Good".
2	Glows Brightly	Short circuit fault
3	If not Glow	Open circuit fault

3. After rectifying all the faults, connect the appliance parallel to the supply and find out the value of current and voltage
   1 Current = _____
   2 Voltage = _____

Result

I have known the method of preparing an appliances test board and also known the method of testing all the appliances by using test appliance board.

And also I have measured the value of current and voltage by ammeter and voltmeter respectively. The value of

1. Current = _____
2. Voltage = _____

EMA_English_Practical.indd 211 11/9/2020 3:56:11 PM