- Run the cable in the PVC pipe as per the wiring diagram.
- Connect the terminals of switches and lamp holder as per the circuit diagram.
- Connect the leads of pendent holder by using wire.
- Fix the lamp in pendent holder.
- Give supply and check the circuit.

Result

I have known the method of one lamp controlled by one regulator. After giving supply to the circuit through one way switch, turn the regulator in clock wise direction and find out the brightness of the lamp.



EMA_English_Practical.indd 215 11/9/2020 3:56:13 PM