Aim

To know and do the wiring connection method of Fluorescent Lamp.


Tools Required

S.No	Name	Quantity
1	Screw Driver	1
2	Electrician Knife	1
3	Cutting Plier	1
4	Poker	1
5	Tester	1

Materials Required

S.No	Name	Quantity
1	Fluorescent Lamp	2
2	LED Tube Light	1
3	Choke	1
4	Starter	1
5	Electronic Choke	1
6	Single Strand Conductor	15 meter
7	Insulation Tape	1
8	Sleeves	10 cm
9	Tube Light Holder	4
10	Starter Holder	1

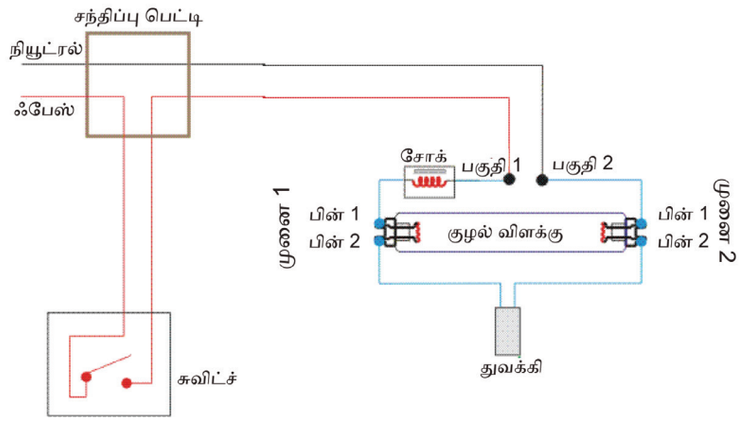Connection of tube light with choke and starter



Procedure

Phase supply is given to the pin 1 of the first terminal through switch and choke (all are connected in series)

Neutral is connected to pin 1 of the second terminal

Pin 2 of the both the terminals are connected to starter.

These connections are shown in the conection diagram

EMA_English_Practical.indd 217 11/9/2020 3:56:13 PM