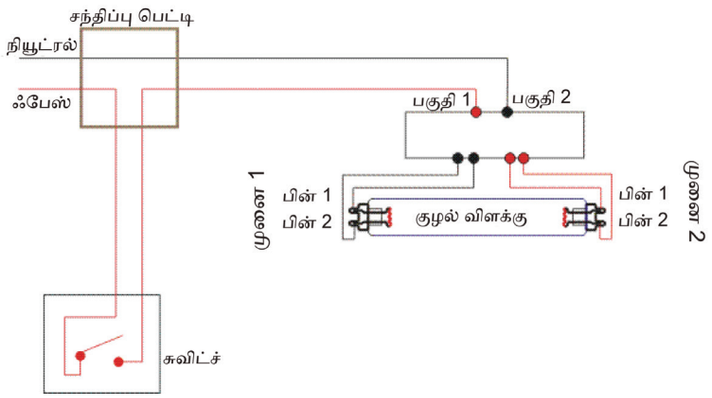
Connection of Tube Light with Electronic Choke




Procedure

Phase supply is given to the input side (L) of the choke through switch.

Neutral is given to the input side (N) of the choke directly.

From choke four wire connections are taken and they are connected to both the terminals as shown in the diagram.

Connection Diagram of LED Tube Light

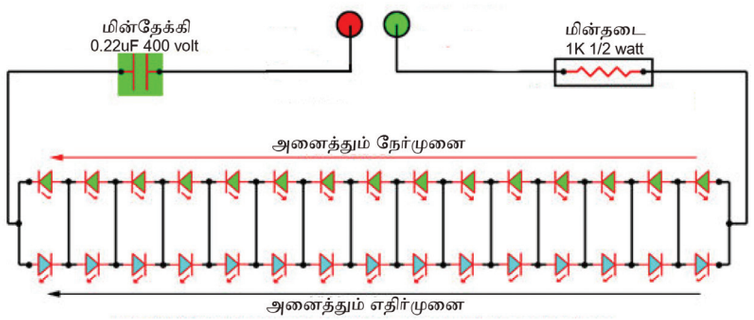

Procedure

As shown in the diagram, phase and neutral supply is given to the LED tube light

Result

Verified and known the method of doing wiring connection of tube light with various chokes.



EMA_English_Practical.indd 218 11/9/2020 3:56:14 PM