Procedure

- Study the layout diagram and the cable route, distance location of fitting of all accessories.
- Draw the wiring connection as per the line diagram.
- List out the materials required for this wiring.
- Confirm how to fix PVC pipe.
- Fix the PVC pipe by using clamps, junction box and switch boxes using wooden screws.
- Run the cable in the PVC pipe as per the wiring diagram.
- Connect the terminals of switches and lamp holder as per the circuit diagram.
- Connect the leads of pendent holder by using wire.
- Fix the lamp in pendent holder.
- Give supply and check the circuit.



Result

I have known the method of doing stair-case wiring. If both switches are in 'UP' or 'DOWN' position, the lamp glows. Otherwise the lamp does not glow.

EMA_English_Practical.indd 222 11/9/2020 3:56:16 PM