Aim

To learn and know about the method of doing Godown wiring.


Tools Required

S No	Name	Quantity
1	Screw Driver	1
2	Cutting Plier	1
3	Tester	1
4	Electrician Knife	1
5	Poker	1
6	Drilling Machine	1
7	Ball Peen Hammer	1
8	Hacksaw Frame	1
9	Measurement Tape	1
10	Try Square	1

Materials Required

S No	Name	Quantity
1	Wooden Board - 3" × 4"	1
2	3/4" P.V.C Pipe	2 length
3	1/18 Copper Wire	12 meter
4	One Way Switch	1
5	Two Way Switch	2
6	Lamp Holder	3
7	Three Way Junction Box	3
8	¾" Clamp	24
9	¾" Screws	48
10	1 ½" Screws	6
11	Insulation Tape	1
12	60W Lamp	3

Layout Diagram

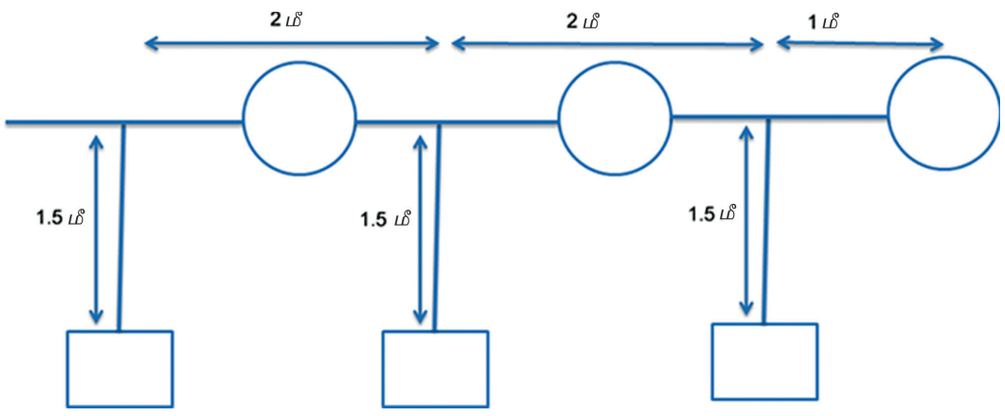

EMA_English_Practical.indd 224 11/9/2020 3:56:17 PM