
Connection Diagram

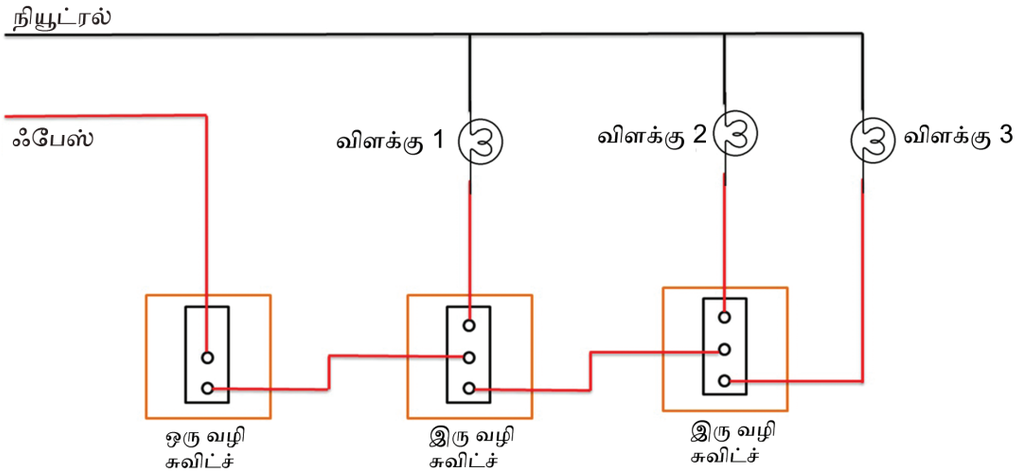

Procedure

- Study layout diagram and the cable route, distance location of fitting of all accessories.
- Draw the wiring diagram as per the line diagram.
- List out the materials required for this wiring.
- Confirm how to fix PVC pipe.
- Fix the PVC pipe by using clamps, junction box and switch boxes by using wooden screws.
- Run the cable in to the PVC pipe as per the wiring diagram.
- Connect the terminals of switches and lamp holder as per the circuit diagram.
- Connect the leads of pendent holder by using wire.
- Fix the lamp in pendent holder.
- Give supply and check the circuit.

Result

I have known the method of doing the godown wiring. If we switch ON the first switch, first lamp only glows. And if we switch ON the second switch, second lamp only glows. And if we switch ON the third switch, third lamp only glows.

EMA_English_Practical.indd 225 11/9/2020 3:56:17 PM