
Connection Diagram

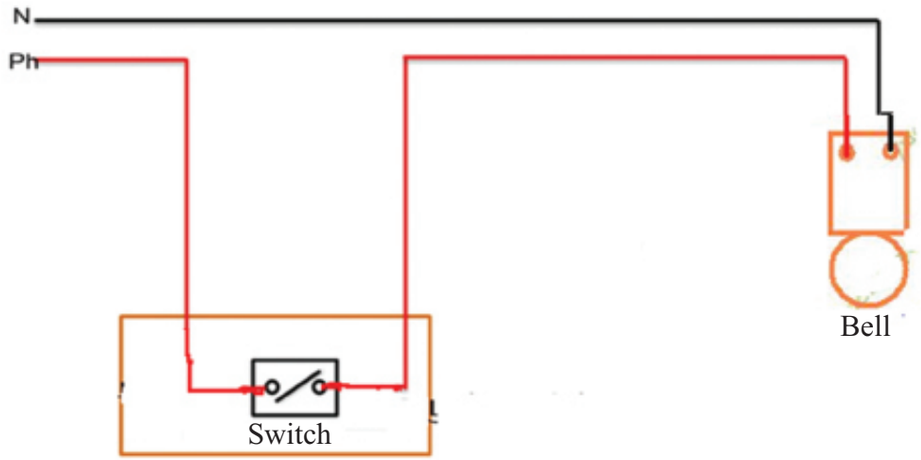


Procedure

- Study the layout diagram, the cable route, distance location of fitting of all other accessories.
- Draw the wiring diagram as per the line diagram.
- List out the materials required for this wiring.
- Confirm how to fix PVC pipe.
- Fix the PVC pipe by using clamps, junction box and switch boxes using wooden screws.
- Run the cable in the PVC pipe as per the wiring diagram.
- Connect the terminals of switches and ceiling rose by using wire as per the circuit diagram.
- Fix the electric bell in ceiling rose.
- Give supply and check the circuit.

Working of an Electric Bell

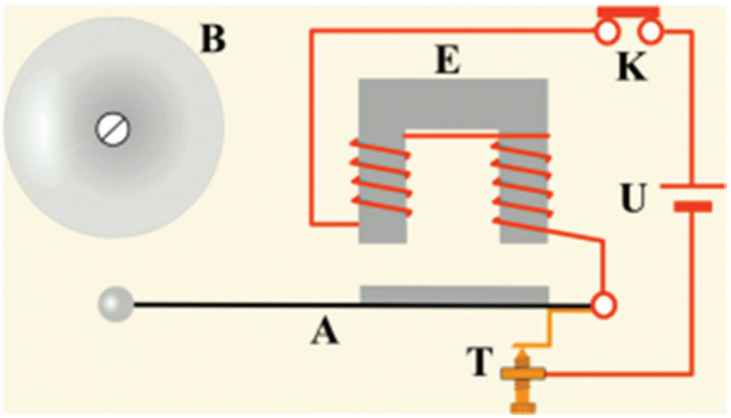The image below shows the internal mechanism of an electric bell.



EMA_English_Practical.indd 228 11/9/2020 3:56:18 PM