The step by step process of the working of the electric bell is described below:

- If the switch is pressed ON and the current will flows through the circuit.
- The electromagnet is powered and generates a magnetic field, that attracts the iron strip towards it.
- The striker of the bell strikes the gong (bell)
- When the striking arm strikes the gong, the contact is broken and current stops flowing through the circuit.
- This causes the electromagnet to lose its magnetic field.
- The connected spring arm returns the striker to its original rest position.
- The contact is restored and current flows through the circuit (provided the main switch is still pressed).
- The process is repeated.

Result

I have known the method of preparing an electric bell controlled by one way bell switch and its working. After giving supply to the circuit, the electric bell will ring.

EMA_English_Practical.indd 229 11/9/2020 3:56:18 PM