PART C

Mark 5

Answer the Questions not Exceeding one page

1. Explain the properties of a conductor.
2. Explain the properties of insulators.
3. Explain the difference between Electromotive force and Potential Difference.
4. What are the important rules for series circuit?
5. What are the important rules for parallel circuit?
6. Three resistors 3Ω,6Ω and 18Ω are connected in parallel. The current flow of the circuit is 3A. Find the value of i)Total Resistance ii)voltage.
7. Explain the laws of Resistors.

PART D

Mark 10

Answer the Questions not Exceeding two page

1. What are the types of conductors Explain.
2. Explain the construction and working of series circuit.
3. Explain the construction and working of parallel circuit.
4. Explain the Kirchoff's Laws.
5. Explain the construction and working principle of condenser.
6. What are the types of capacitors? Explain.

Reference Book

1. A text book of Electrical Technology' Volume I by B.L. Theraja and A.K. Theraja, S. Chand & Company Ltd.

Internet Resource

www.stevespanglerscience.com

EMA_English_Chp02.indd 37 11/9/2020 2:44:52 PM