In Delta Connection

Phase voltage = Line Voltage

$$V_{ph} = V_L$$

$$\text{Phase current} = \frac{\text{Line current}}{\sqrt{3}}$$

$$I_{ph} = \frac{I_L}{\sqrt{3}}$$


Both in star and Delta connection in three phase system

Power $p = \sqrt{3} V_L I_L \cos\theta$

Digital energy meters displayed the energy consumption accurately.

Activities

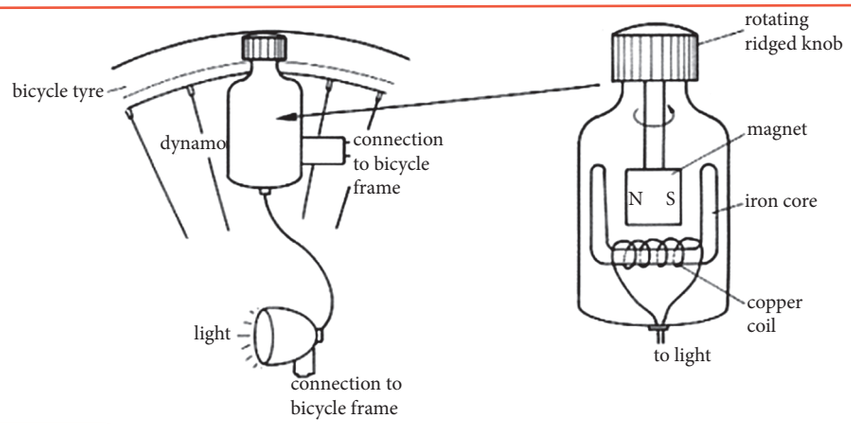1. Practice the following (dynamo) type of voltage generation.



GLOSSARY

AC Supply	—	மாறுதிசை மின்சாரம்
Frequency	—	அலைவு வேகம்
Average Value	—	சராசரி மதிப்பு
Peak Value	—	உச்சமதிப்பு
Time Period	—	கால அளவு
Instantaneous Value	—	கன மதிப்பு
Effective Value	—	பயன் மதிப்பு
Form Factor	—	வடிவுக்காரணி
Peak Factor	—	உச்சக்காரணி
Power Factor	—	திறன்காரணி
Voltage Sensor	—	மின்னழுத்த உணர்வி
Current Sensor	—	மின்னோட்ட உணர்வி

EMA_English_Chp05.indd 85 11/9/2020 3:09:16 PM