PART A

Mark 1

Choose the Correct Answer:

1. The unit of the flux density is
   a) Ampere b) Volt
   c) Weber d) Weber/m_2

2. The unit of the frequency is
   a) Henry b) Hertz
   c) Cycles d) Ampere

3. The value of form factor is
   a) $2/\pi$ b) $\pi/2$
   c) 1.414 d) 1.11

4. The value of peak factor is
   a) $2/\pi$ b) $\pi/2$
   c) 1.414 d) 1.11

5. In the value of power factor, which is incorrect
   a) Unity b) 0.8 leading
   c) 0.8 lagging d) 1.5

6. Power factor of pure resistive circuit is
   a) Unity b) Leading
   c) lagging d) None of the above

7. Power factor of pure Inductive circuit, with respect to current is
   a) unity b) leading
   c) lagging d) none of the above

ST5DB5

8 Power factor of pure capacitive circuit, with respect to current is
   a) unity b) leading
   c) lagging d) none of the above

9. The unity of Inductance is
   a) Henry b) Hertz
   c) Farad d) Ohm

10. The unit of capacitance is
   a) Henry b) Hertz
   c) Farad d) Ohm

11. The unit of Impedance
   a) Henry b) Hertz
   c) Farad d) Ohm

12. The unit of Capacitive reactance and Inductive reactance is
   a) Henry b) Hertz
   c) Farad d) Ohm

13. Inductive reactance X_L is equal to
   a) $2\pi fc$ b) $1/2\pi fc$
   c) $2\pi fl$ d) $1/2\pi fl$

EMA_English_Chp05.indd 86 11/9/2020 3:09:16 PM