PART A

Mark 1

Choose the Correct Answer:

14. Capacitive reactance X_C is equal to
    a) $2\pi fc$ b) $1/2\pi fc$
    c) $2\pi fl$ d) $1/2\pi fl$

15. Star connection is also known
    a) Delta b) Y
    c) Mesh d) None of the above

16. Delta connection is also known as
    a) Star b) Y
    c) Mesh d) None of the above

17. X_L denotes
    a) Resistance
    b) Inductive reactance
    c) Capacitive reactance
    d) Impedance

18. X_C denotes
    a) Resistance
    b) Inductive reactance
    c) Capacitive reactance
    d) Impedance

19. Four wire system can be obtained from
    a) Series connection
    b) Parallel connection
    c) Star connection
    d) Delta connection

20. In three phase, phase difference is
    a) 90^o b) 180^o
    c) 120^o d) 360^o

21. In star connection, phase current Iph is equal to
    a) V_L b) I_L
    c) Vph d) $\frac{I_L}{\sqrt{3}}$

22. In Delta connection, phase voltage Vph is equal to
    a) V_L b) I_L
    c) Vph d) $\frac{I_L}{\sqrt{3}}$

23. Digital energy meters are used for the following reason
    a) High accuracy
    b) Small size
    c) Long life
    d) All of the above

EMA_English_Chp05.indd 87 11/9/2020 3:09:16 PM