PART C

Mark 5

Answer the Questions not Exceeding one page

1. Explain the power factor with vector diagram.
2. Briefly explain the AC circuit which is having only resistance.
3. Briefly explain the AC circuit which is having only Inductance.
4. Briefly explain the AC circuit which is having only capacitance.
5. Explain the reasons for the use of three phase system over single phase system.
6. What are the advantages of star connection over Delta connected system?
7. What are the advantages of digital energy meter?

PART D

Mark 10

Answer the Questions not Exceeding two page

1. Explain RLC series circuit with neat diagram.
2. Explain the star connection of three phase system with neat diagram.
3. Explain the Delta connection of three phase system with neat diagram.
4. Explain how alternating current and voltage is generated with neat diagram.

Reference Book

1. 'A text book of Electrical Technology' Volume I, by B.L. Theraja and A.K. Theraja, S. Chand & Company Ltd.

Internet Resource

www.allaboutcircuits.com

EMA_English_Chp05.indd 89 11/9/2020 3:09:16 PM