
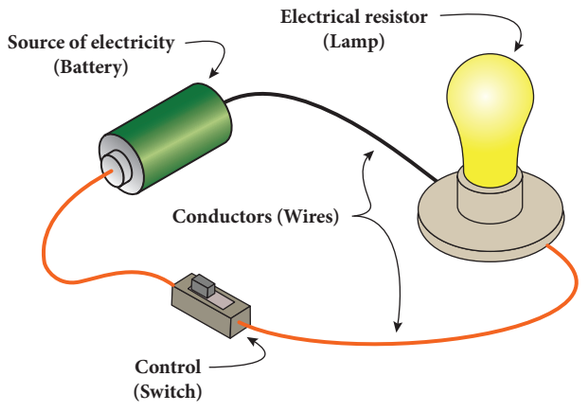


Figure 5.12 Simple electric circuit

The above figure shows a simple circuit containing a battery, two wires, key and an electric bulb. The source can be a battery or the electric outlet in your room. The electrical resistor refers to the device that consumes the energy. Control (key) is the mechanism that is used to start, stop and regulate the electric current. When the key is on, electrons from the battery flow through the circuit from the negative terminal through the wire conductor, then through the bulb and finally back to the positive terminal. The light glows when current is flowing through its filament. There are two basic ways in which we can connect these components. They are: series and parallel.

DO YOU KNOW?

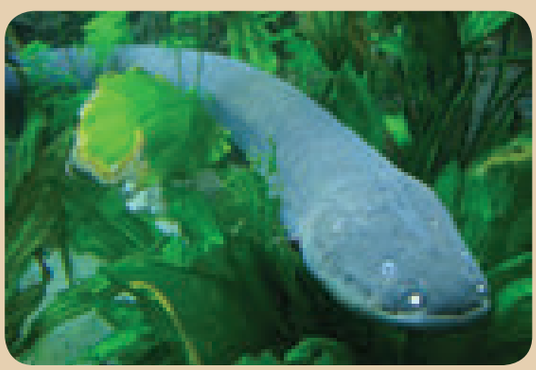The electric eel is a species of fish which can give electric shocks of upto six hundred fifty watts of electricity. But if the eel repeatedly shocks, its electric organs become completely discharged. Then a person can touch it without being shocked.



5.7.1 Series Circuit

A series circuit is one that has more than one resistor (bulb) but only one path through which the electrons can travel. From one end of the battery the electrons move along one path with no branches through the resistors (bulbs) to the other end of the cell. All the components in a series circuit are connected end to end. So, current through the circuit remains same throughout the circuit. But, the voltage gets divided across the bulbs in the circuit. In the following series circuit two bulbs are used as resistors.

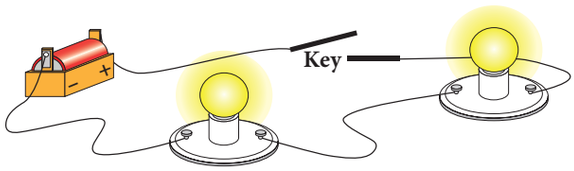


Figure 5.13 Series circuit

In this series circuit, charges (electrons) from the battery have only one path to travel. Here battery, key and two bulbs are connected in series. Charges flow from the battery to each bulb, one at a time, in the order they are wired to the circuit. If one bulb in the circuit is unscrewed, the current flow to another bulb would be interrupted. We put serial lights during festivals. If the lights are in a series circuit, one burned out bulb will keep all the lights off. If the number of bulbs in a circuit with a battery increases, the light will be dimmer because many resistors are acting on the same power from the battery.

We saw that in series circuit same current travels through every resistance and the voltage will be different across each resistance. Let us consider three bulbs connected in series. Let I be the current through the circuit and V_1, V_2, V_3 be the voltage across each bulb. The supply voltage V is the total of the individual voltage drops across the resistances (bulbs).

$$V = V_1 + V_2 + V_3$$

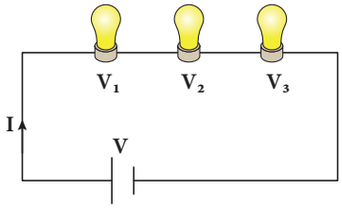


Figure 5.14 Voltage in series circuit

8th_Science_Unit-5_EM.indd 53 21-02-2020 16:44:32